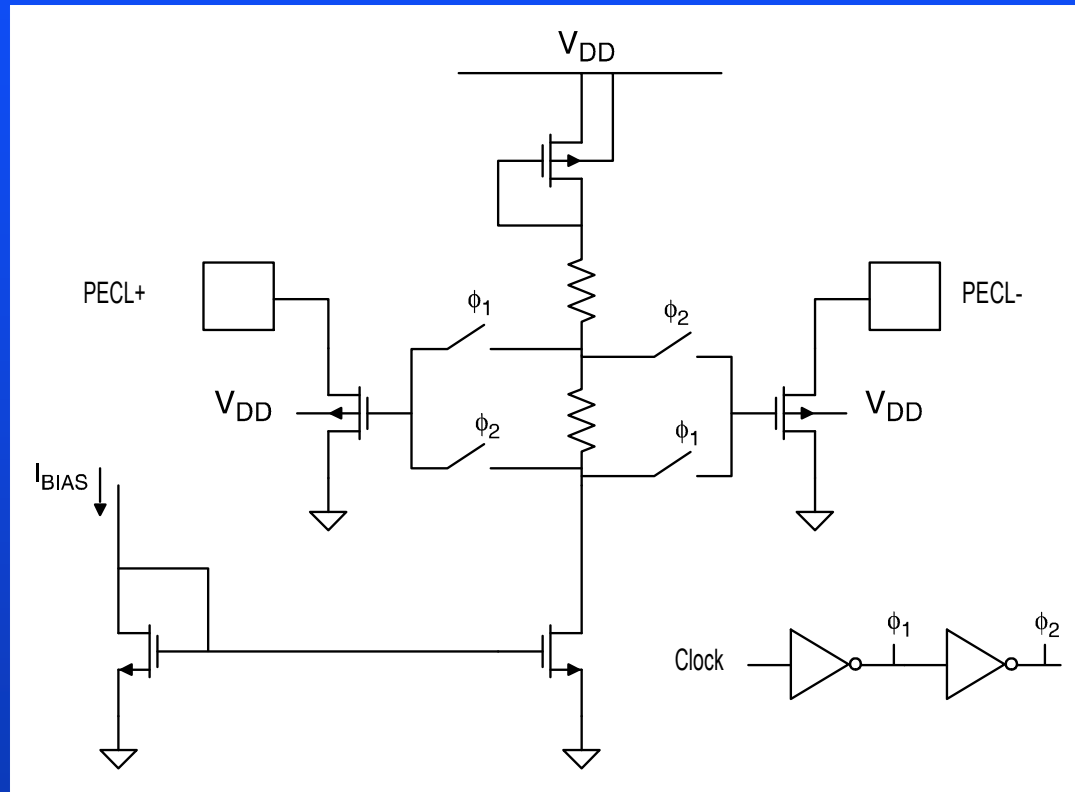



Successful Design Looks Beyond the Schematic

PECL in a PICKLE



Pseudo ECL Driver (PECL) Schematic



 PECL Output Simulations: SPICE from Schematics



PECL Outputs in Silicon

  


BAD

What went wrong???


Candidate Answers

- **SPICE**
- **SPICE Models**
- **Charge feedthrough from switches**
- **Package lead inductance**
- **Package interlead mutual inductance**
- **Some other parasitic??**

 Layout of PECL **Bias** and PECL input **Clock**



PECL Output with 5fF coupling!!

 

Lessons Learned

- **TAKE CARE WITH ALL BIAS LINES!**
 - Shield them from stuff below
 - Shield them from stuff above
 - Shield them from stuff beside


How small is small?

A 8-Bit SAR Case Study

■ Description


- 8-Bit SAR A/D Converter
- 0.35 μm CMOS Double-Poly, Quad Metal
- Array used “bridge capacitor” technique
- Unit Capacitor was ~ 48 fF ($7\mu\text{m} \times 7\mu\text{m}$)

8-Bit Capacitor Array

 


Unit capacitor is 48 fF

Capacitor Array

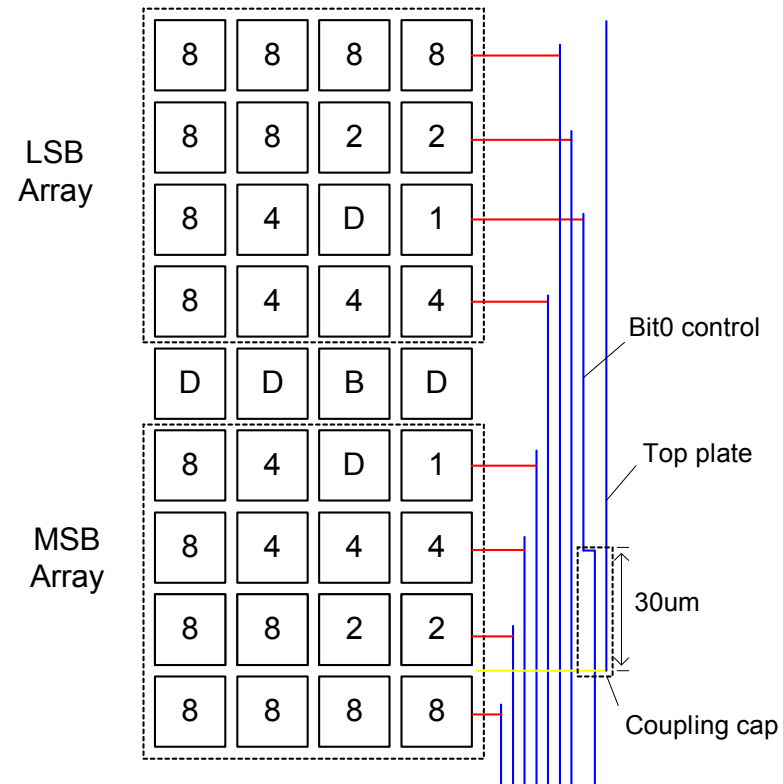

View shows
top plate
only


Capacitor Array

 

Parasitic coupling is **MAGNIFIED** across the bridge capacitor and thus for 48 fF unit capacitors a 3 fF parasitic coupling capacitor is magnified by 16! This **DOUBLES** the weight of Bit0!!! Thus 3fF changes an 8-bit converter to a 7-bit converter.


Does Plastic Change Your Life?

Coupling Varies with Dielectric

 

Before plastic encapsulation, the fringe extends into free air ($\epsilon \sim 1$)

Coupling Varies with Dielectric

 


After plastic encapsulation, the fringe extends into plastic ($\epsilon > 1$, perhaps 3?)

Additional Solution: Metal Shield

- **As much of the capacitor area as possible should be covered with metal.**
- **This caused the fringe fields to terminate on the “shield” (the metal covering) and not on adjacent capacitors. Because this was a single-metal process the coverage was not perfect.**
- **In today’s multi-metal processes, using one layer as a shield plate is easy.**


The Whole Chip Oscillates!

The Circuit

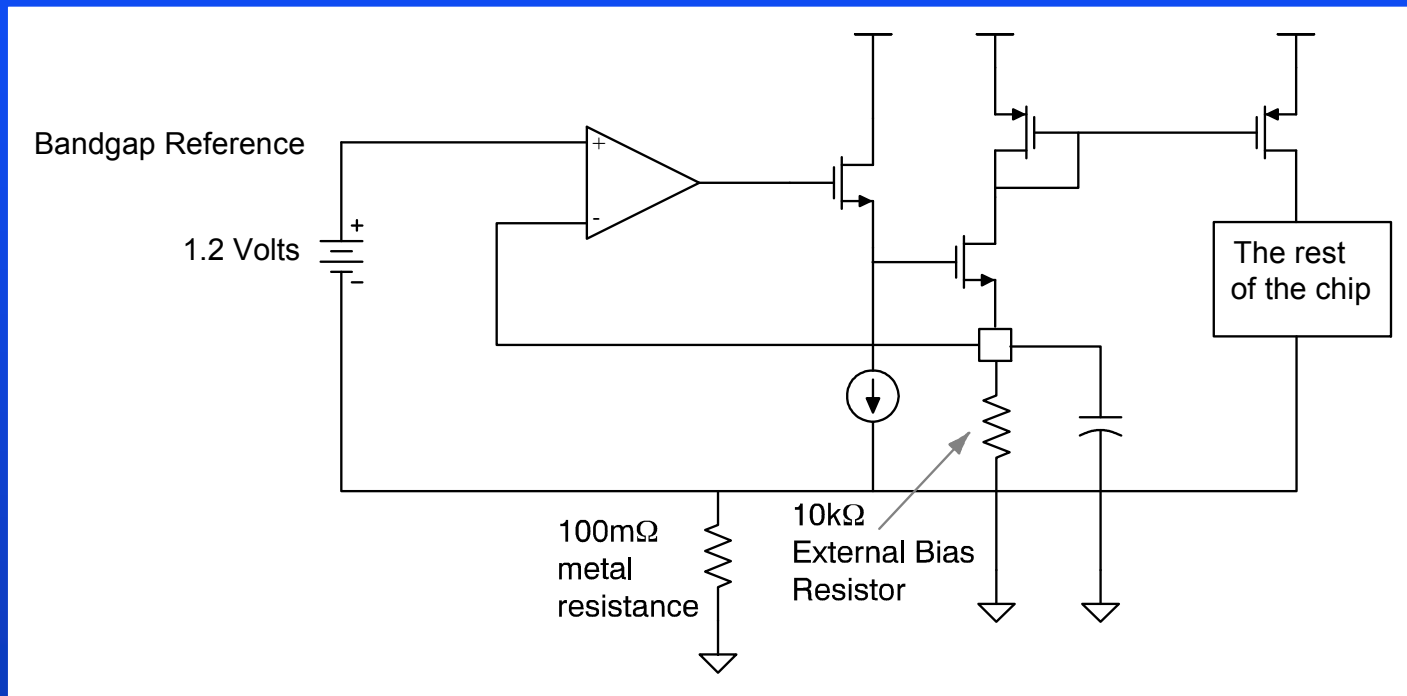


Laboratory Observations

Bias
Pin
→

 

Spice Simulation

Bias
Pin

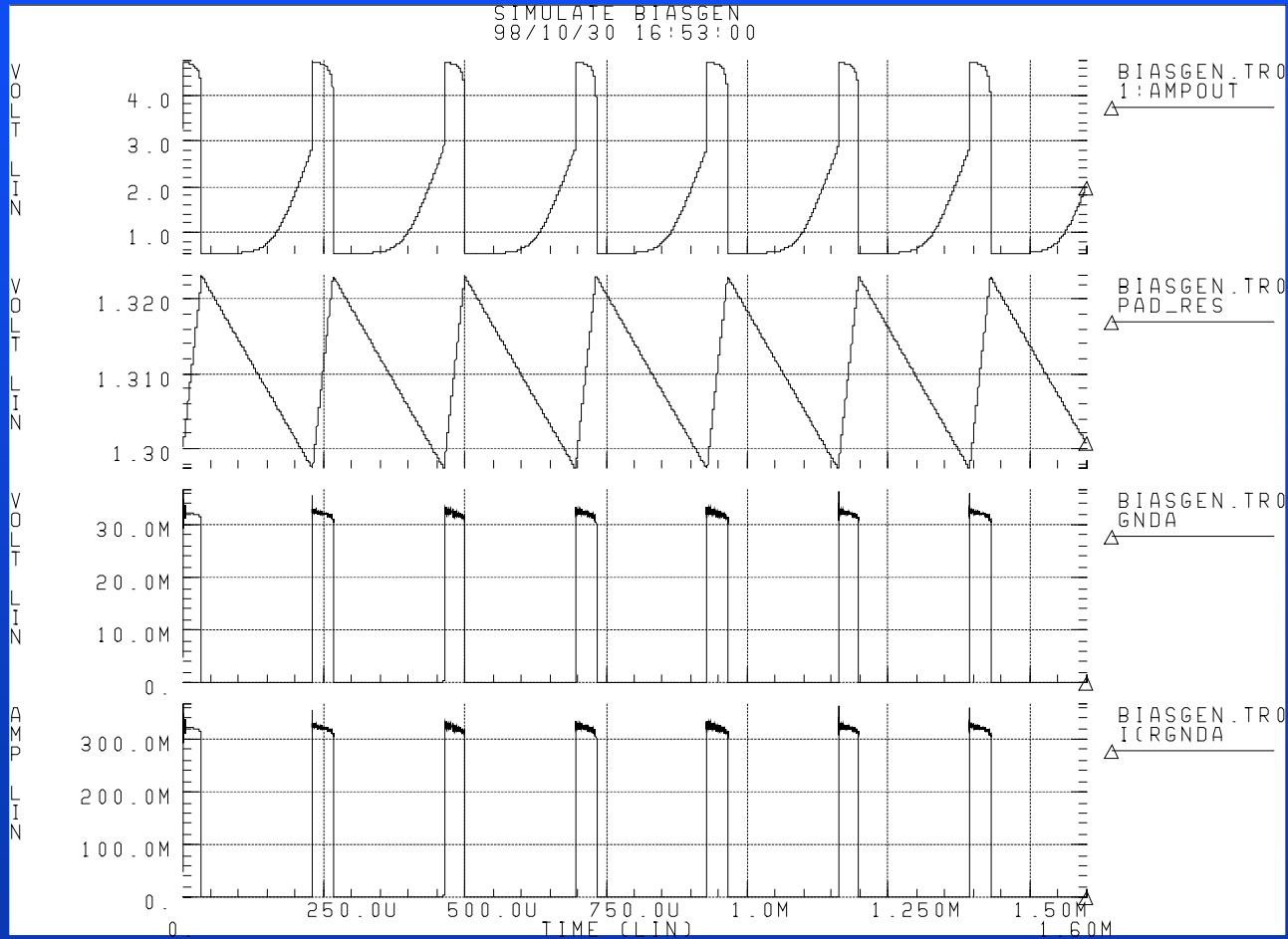

The Moral of the Story...


- Watch out for BIG feedback loops
- Dont always ignore $100\text{m}\Omega$ of metal

***“You Don’t Miss the Water ‘til the Well
Runs Dry”***


Parasitic Bipolars

- In a Bandgap Reference design, it was discovered that a P+ resistor string was lying inside an N-Well which was floating.
- Is that a problem?

The Circuit (w/o Parasitics)

 

The Circuit (w/ Parasitics)

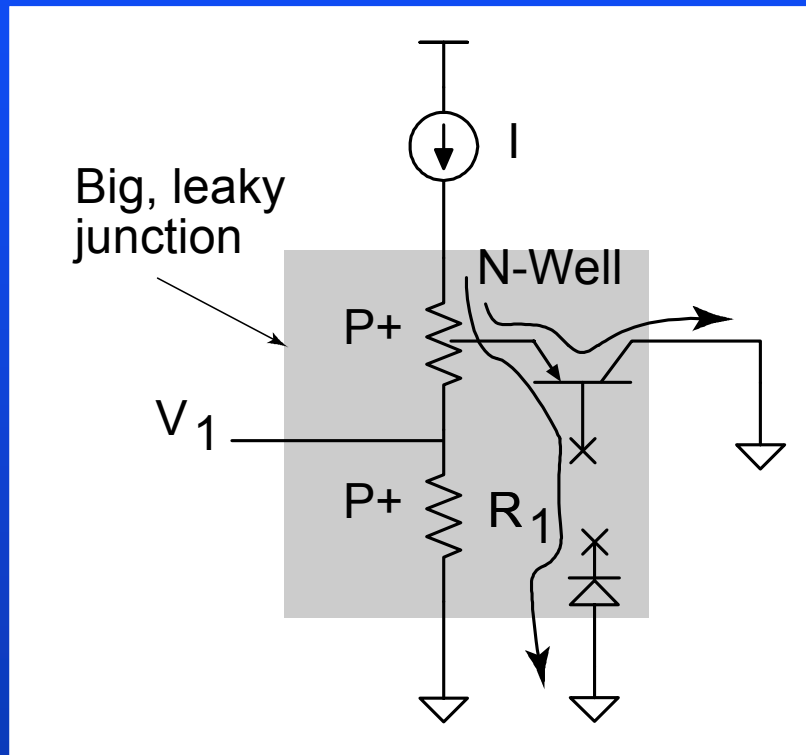

↑
Temp.

↑
Leakage


The Moral of the Story

- Think about where your N-Well is connected.
- Use three-terminal resistors!!!
 - This forces you to think!


Remember Christian Huygens

Coupled Oscillators

The Circuit

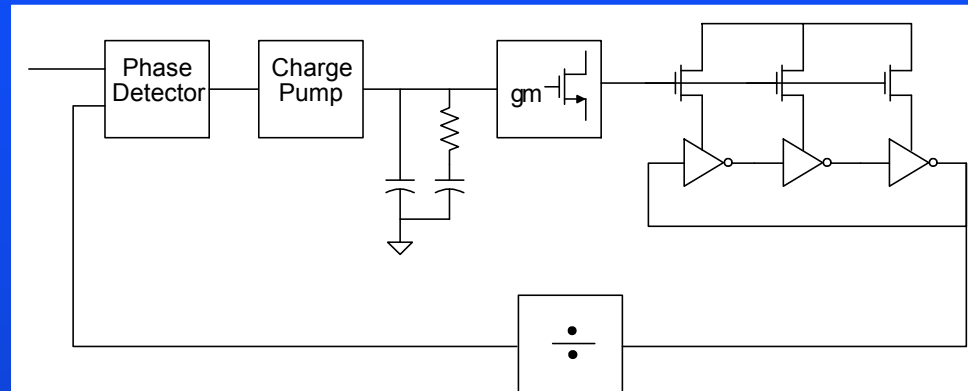


Synthesizer with VCO

 


Clock Recovery DAC and VCO

 Transfer Function of CR VCO Measured in the Lab




Layout of Two VCOs

 

Layout Detail

Separation
approx: 1.5mm

 

Solution

- **Separate VCOs with distance**
- **Reduce substrate coupling path with improved layout**

The Clock Experiment




Matching Principles

Matching Principles

- **Unit Replication**
- **Yiannoulos-Path**
- **Uniform Perimeters**
- **Avoid hard corners for capacitors**
- **Common Centroid**
- **Photolithographic Invariance**
- **The same means *the same***

Unit Replication Principle

Capacitor Example

 

Total capacitance has an area and a perimeter component

Perimeter/Area Ratio


$$C_1 = C_{1A} + C_{1P}$$

$$C_2 = C_{2A} + C_{2P}$$

$$\frac{C_2}{C_1} = \frac{C_{2A} + C_{2P}}{C_{1A} + C_{1P}} = \left[\frac{C_{2A}}{C_{1A}} \right] \left[\frac{1 + \frac{C_{2P}}{C_{2A}}}{1 + \frac{C_{1P}}{C_{1A}}} \right]$$

Match C_P/C_A to force the overall ratio to the area ratio.

Unit Replication

 

Both areas and perimeters are matched!
1:4 ratio for perimeters, 1:4 ratio for areas

Unit Replication

- The Unit Replication Principle applies to:
 - Capacitors
 - Transistors
 - Resistors

USE IT!



Non-Unit Ratios

- **What do you do if you need a ratio that requires a non-unit ratio? (I.e., What do you do if the size of a unit capacitor for the particular ratio desired is too small to use the unit matching technique.)**
- **E.g., 1:4.1; Unit cap is 10fF. You cannot build an 0.1fF cap.**

Rule: Don't use "i.e." when you mean "e.g."

Solution: The Yiannoulos¹-Path Technique

Example: Desired Ratio - 13.8:14

 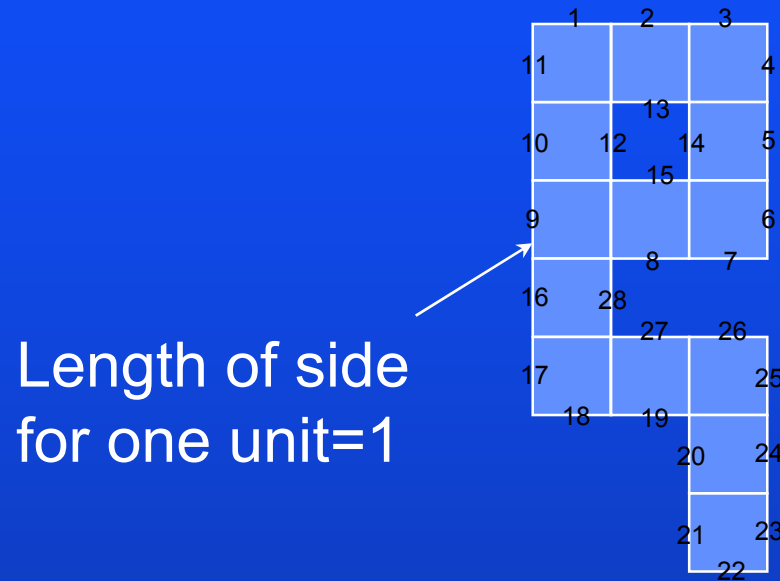

Length of side=0.8

Ratio of areas: 14:13.8


Ratio of perimeters: 28:27.6

Amazing!

1. Aristedes A. Yiannoulos


Uniform Perimeter Principle

Capacitor Example

 

How accurate is the 1:4 ratio given the perimeter difference?

Uniform Perimeter Principle

 

The perimeter of every unit is the same.


USE IT!

Uniform Perimeter Principle

- Imagine yourself as being really small.
- Stand at the center of a unit component and peer in all directions.
- If you cannot determine which unit component you are standing on, then you have properly applied the *Uniform Perimeter Principle*.

How far out do you have to match? Just far enough!

Avoid Hard Corners for Capacitors

 

Why?

Consider a Circle vs. Square

$$A_{circle} = \pi r^2$$

$$A_{square} = d^2$$

$$\text{if } A_{circle} = A_{square}$$


$$r = \frac{d\sqrt{\pi}}{\pi}$$

$$\frac{P_{circle}}{P_{square}} = \frac{2\sqrt{\pi} d}{4d} = \frac{\sqrt{\pi}}{2} < 1$$

Perimeter effects are minimized

Common Centroid Principle

Transistor Example

 

$$V_{TA} < V_{TB} < V_{TC}$$

Thus:

$$I_{BC} < 2I_A$$



Common Centroid Principle


$$V_{TB} < V_{TA} < V_{TC}$$

$$(1/2)(V_{TC} + V_{TB}) = V_{TA}$$


Thus:

$$I_{BC} = 2I_A$$

to a first-order approximation

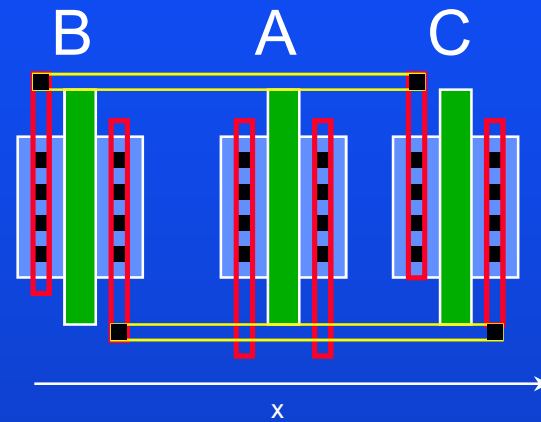


Photolithographic Invariance Principle

 



Because of implant angle, polysilicon casts a shadow on to drain/source region.

Photolithographic Invariance Principle

 

The Same IS The Same

  - Unit matching requires that every aspect of things being matched are the same.
- For MOSFETs, this means metal coverage as well!



Transistors A and B
are NOT matched!


Metal Coverage Issues

- **For critical matching, do not cover matching transistors with metal.**
- **For less critical matching, at least cover the matched transistors in the same way.**


Package Parasitics

Picking Proper Package Pinout

Typical Plastic Package Cross Section

 

LCC Package

 


LCC Package Parasitics

LCC Package Data

Lead Count	Electrical parameter			
	R (mΩ)	L (nH)	C _L (pF)	C _{LL} (pF)
20 square	68 - 78	3.5 - 6.3	0.8 - 0.9	0.3 - 0.4
28 square	68 - 78	3.7 - 7.8	1.0 - 1.1	0.4 - 0.5
28 rectangle	68 - 78	3.3 - 4.2	0.6 - 0.7	0.2 - 0.3
32 rectangle	68 - 78	3.9 - 5.8	0.8 - 1.1	0.1 - 0.6
44 square	68 - 78	4.3 - 6.1	1.1 - 1.4	0.2 - 0.8
52 square	68 - 78	6.1 - 8.4	1.0 - 1.3	0.2 - 0.8
68 square	68 - 78	5.3 - 8.9	1.4 - 2.0	0.2 - 1.0
84 square	68 - 78	8.4 - 10.8	1.8 - 2.7	0.25 - 1.2

Note: C_L is load capacitance and C_{LL} is lead-to-lead capacitance

QFP Package

 


QFP Package Parasitics

QFP Package Data				
Lead Count	Electrical parameter			
	R (mΩ)	L (nH)	C _L (pF)	C _{LL} (pF)
84	70-80	5.8 - 6.6	< 1.0	< 0.5
100	70-80	6.1 - 7.1	< 1.5	< 1.0
132	70-80	7.3 - 8.5	< 2.0	< 1.5
164	70-80	8.0 - 14.5	< 2.2	< 1.5
196	70-80	9.0 - 15.5	< 1.5	< 1.6


Note: C_L is load capacitance and C_{LL} is lead-to-lead capacitance

Typical QFP Leadframe

 


Pin 1


PQFP Pin-Pin Mutual Inductance

 

PQFP Self Inductance

 


TBGA CONSTRUCTION

 

NOT TO SCALE

TBGA

 

NOT TO SCALE

TBGA vs PBGA


ELECTRICAL COMPARISON

Measured and Modeled Data

	INDUCTANCE (nH)				CAPACITANCE (pF)				
	Corner		Center		Corner		Center		
	<u>L11</u>	<u>L12</u>	<u>L11</u>	<u>L12</u>	<u>C11</u>	<u>C12</u>	<u>C11</u>	<u>C12</u>	
256 PBGA									
■ Measured	6.4	0.3	1.8	0.3	1.1	<0.1	0.7	<0.1	
■ Modeled	6.5	0.4	2.0	0.8	1.0	<0.1	0.4	<0.1	
256 TBGA									
■ Measured	9.0	3.0	3.5	1.2	1.0	0.5	0.9	0.3	
■ Modeled	9.1	2.5	3.7	1.3	1.0	0.3	0.9	0.1	
352 TBGA									
■ Measured	10.0	2.0	3.6	0.8	1.3	0.2	1.1	0.1	
■ Modeled	10.4	2.1	3.4	0.9	1.0	<0.1	0.4	<0.1	


*256=27x27mm / **352=35x35mm

PBGA DESIGN

 

NOT TO SCALE

PBGA MULTI-CHIP MODULE

 


NOT TO SCALE

Minimize Sensitivity to Package Inductance


- Take advantage of orthogonality.
- Keep noisy digital currents in pins far away from sensitive analog input pins.
- Use shortest pins for circuits requiring lowest inductance.
- Force opposing loop currents

Take Advantage of Orthogonality

BAD

 


GOOD

 


In most cases you are probably OK to place offending pins on opposite sides of the package if the package is large enough.

Force Opposing Currents

BAD

 


BETTER

 

Opposing
loops cancel

Force Opposing Currents

BETTER YET

 

Orthogonality plus opposing currents

THE END